



**DEPARTMENT OF ELECTRONICS AND  
TELECOMMUNICATION  
ENGINEERING, IIIT BHUBANESWAR**

# **VLSI LAB RECORD**

**SUBMITTED BY:  
SUDIP NAYAK**

**B. Tech (3rd YEAR, 6TH SEMESTER, B220061)**

# C O N T E N T S

EXPT. NO.	TITLE	PAGE NO.
<b>1</b>	Various Logic Gates in Verilog using Structural and Data Flow Modelling	3-5
<b>2</b>	Half Adder and Full Adder in Verilog Using Structural and Data Flow Modelling	6-11
<b>3</b>	8 Bit Adder Using Structural Verilog	12-13
<b>4</b>	4 Bit Multiplier Using Structural Verilog	14-16
<b>5</b>	3:8 Decoder and 8:3 Encoder Using Behavioral Modelling	17-20
<b>6</b>	Latches & Flip Flops in Verilog	21-26
<b>7</b>	Shift Registers (SISO, SIPO, PISO, PIPO)	27-32
<b>8</b>	Universal Shift Register	33-35
<b>9</b>	4-bit Counters	36-38
<b>10</b>	PRBS Generator	39-40

# EXPERIMENT 01

## AIM

In this experiment, our aim was to simulate various logic gates (AND, OR, XOR) in Verilog using both Structural and Data Flow Modelling.

## SOFTWARE USED

Vivado 2018.3

## STRUCTURAL MODELLING

### VERILOG CODE

```
`timescale 1ns / 1ps


module SM61(
    input A1,
    input B2,
    output andOut1,
    output orOut1,
    output xorOut1
);
    and a3(andOut1, A1, B2);
    or o3(orOut1, A1, B2);
    xor x3(xorOut1, A1, B2);
endmodule
```

### TESTBENCH


```
`timescale 1ns / 1ps

module StructuralTestBench61;
    reg A1, B2;
    wire andOut1, orOut1, xorOut1;
    SM61 sm(.A1(A1), .B2(B2), .andOut1(andOut1), .orOut1(orOut1), .xorOut1(xorOut1));
    initial begin
        A1 = 0 ; B2 = 0 ;
        #10
        A1 = 0 ; B2 = 1 ;
        #10
        A1 = 1 ; B2 = 0 ;
        #10
        A1 = 1 ; B2 = 1 ;
    end
endmodule
```

## WAVE WINDOW OUTPUT

 

## SCHEMATIC

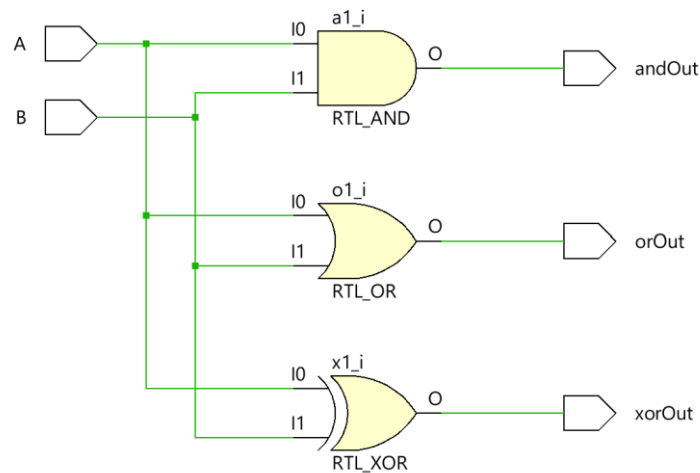

## DATA FLOW MODELLING

### VERILOG CODE

```

`timescale 1ns / 1ps

module SM61(
    input A2,
    input B3,
    output andOut1,
    output orOut1,
    output xorOut1
);
    assign andOut1 = A2 & B3 ;
    assign orOut1 = A2 | B3 ;
    assign xorOut1 = A2 ^ B3 ;
endmodule

```

## TESTBENCH


```

`timescale 1ns / 1ps


module BehaviouralTestBench22;
reg A2, B3;
wire andOut1, orOut1, xorOut1;
SM61 bm(.A2(A2), .B3(B3), .andOut1(andOut1), .orOut1(orOut1), .xorOut1(xorOut1));
  initial begin
    A2 = 0 ; B3 = 0 ;
    #10
    A2 = 0 ; B3 = 1 ;
    #10
    A2 = 1 ; B3 = 0 ;
    #10
    A2 = 1 ; B3 = 1 ;
  end
end
endmodule

```

## WAVE WINDOW OUTPUT

 

## SCHEMATIC

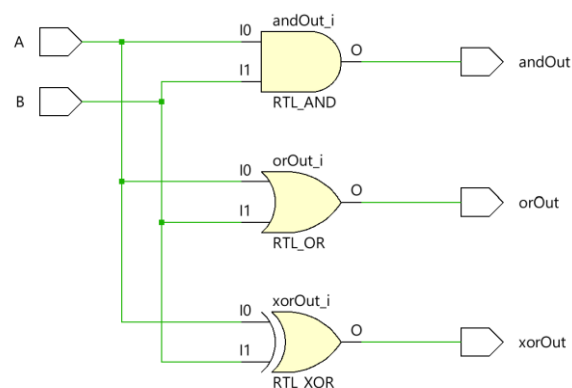

## CONCLUSION

Hence, we successfully simulated various logic gates in Verilog using both structural and data flow modelling and observed the waveforms and schematic.

## **EXPERIMENT 02**

### **AIM**

In this experiment, our aim was to implement half adder and full adder in Verilog using both Structural and Data Flow modelling.

### **SOFTWARE USED**

Vivado 2018.3

### **HALF ADDER USING STRUCTURAL MODELLING**

### **VERILOG CODE**

```
`timescale 1ns / 1ps


module SM61(
    input Am,
    input Bn,
    output Sp,
    output Co
);
    xor x3(Sp, Am, Bn);
    and a3(Co, Am, Bn);
endmodule
```

### **TESTBENCH**


```
`timescale 1ns / 1ps

module StructuralTestBench;
    reg Am, Bn;
    wire sum, carry;
    SM44 sm(.Am(Am), .Bn(Bn), .Sp(sum), .Co(carry));
    initial begin
        Am = 0 ; Bn = 0 ;
        #10
        Am = 0 ; Bn = 1 ;
        #10
        Am = 1 ; Bn = 0 ;
        #10
        Am = 1 ; Bn = 1 ;
    end
endmodule
```

### **WAVE WINDOW OUTPUT**

 

## SCHEMATIC

 

## HALF ADDER USING DATA FLOW MODELLING

### VERILOG CODE

```
`timescale 1ns / 1ps

module DM61(
    input A1,
    input B2,
    output S3,
    output C4
);
    assign S3 = A1 ^ B2 ;
    assign C4 = A1 & B2 ;
endmodule
```

### TESTBENCH

```
`timescale 1ns / 1ps


module DataFlowTestBench12;
    reg A1, B2;
    wire sum, carry;
    DM44 dm(.A1(A1), .B2(B2), .S3(sum), .C4(carry));
    initial begin
        A1 = 0 ; B2 = 0 ;
    end
endmodule
```

```


#10
A1 = 0 ; B2 = 1 ;
#10
A1 = 1 ; B2 = 0 ;
#10
A1 = 1 ; B2 = 1 ;
end
endmodule

```

## WAVE WINDOW OUTPUT

 

## SCHEMATIC

 

## FULL ADDER USING STRUCTURAL MODELLING

## VERILOG CODE

```

`timescale 1ns / 1ps

module SM61(
    input Aa,
    input Bb,
    input Cin,
    output Ss,
    output Cout
);
    wire a1, a2, x1 ;
    xor xor1(x1, Aa, Bb);
    xor xor2(Ss, x1, Cin);
    and and1(a1, x1, Cin);
    and and2(a2, Aa, Bb);

```



```

    or or1(Cout ,a1, a2) ;
endmodule

```

## TESTBENCH


```

`timescale 1ns / 1ps


module StructuralTestBenchhh;
reg Aa, Bb, Cin;
wire sum, carry;
SM44 sm(.Aa(Aa), .Bb(Bb), .Cin(Cin), .Ss(sum), .Cout(carry));
    initial begin
        Aa = 0 ; Bb = 0 ; Cin = 0 ;
        #10
        Aa = 0 ; Bb = 0 ; Cin = 1 ;
        #10
        Aa = 0 ; Bb = 1 ; Cin = 0 ;
        #10
        Aa = 0 ; Bb = 1 ; Cin = 1 ;
        #10
        Aa = 1 ; Bb = 0 ; Cin = 0 ;
        #10
        Aa = 1 ; Bb = 0 ; Cin = 1 ;
        #10
        Aa = 1 ; Bb = 1 ; Cin = 0 ;
        #10
        Aa = 1 ; Bb = 1 ; Cin = 1 ;
    end
endmodule

```

## WAVE WINDOW OUTPUT

 

## SCHEMATIC

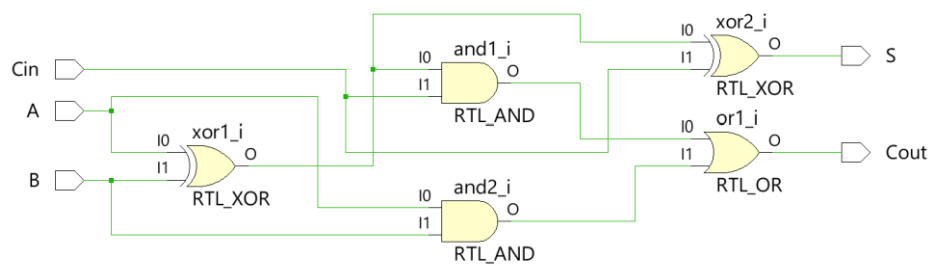

## FULL ADDER USING DATA FLOW MODELLING

### VERILOG CODE

```
`timescale 1ns / 1ps

module DM6(
    input Ai,
    input Bi,
    input Cin,
    output Si,
    output Cout
);
    assign Si = Ai ^ Bi ^ Cin ;
    assign Cout = ((Ai ^ Bi) & Cin) | (Ai & Bi) ;
endmodule
```

### TESTBENCH


```
`timescale 1ns / 1ps
module DataFlowTestBench45;
reg At, Bt, Cin;
wire sum, carry;
DM61 dm(.At(At), .Bt(Bt), .Cin(Cin), .St(sum), .Cout(carry));
initial begin
    At = 0 ; Bt = 0 ; Cin = 0 ;
    #10
    At = 0 ; Bt = 0 ; Cin = 1 ;
    #10
    At = 0 ; Bt = 1 ; Cin = 0 ;
    #10
    At = 0 ; Bt = 1 ; Cin = 1 ;
    #10
    At = 1 ; Bt = 0 ; Cin = 0 ;
    #10
    At = 1 ; Bt = 0 ; Cin = 1 ;
    #10
    At = 1 ; Bt = 1 ; Cin = 0 ;
    #10
```

```


    At = 1 ; Bt = 1 ; Cin = 1 ;
end
endmodule

```

## WAVE WINDOW OUTPUT

 

## SCHEMATIC

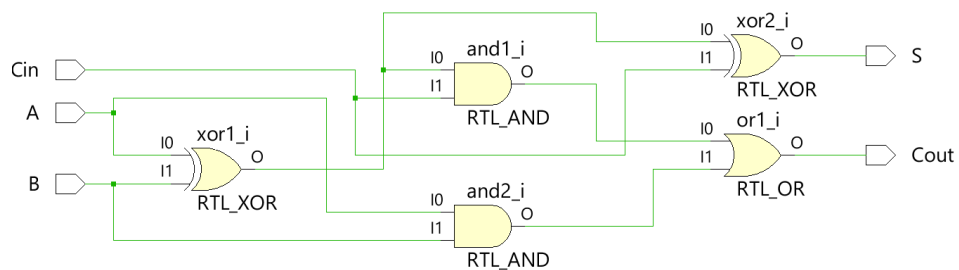

## CONCLUSION

Hence in this experiment, we successfully implemented half adder and full adder using both structural and data flow modelling in Verilog.

## **EXPERIMENT 03**

### AIM

In this experiment, our aim is to implement an 8-bit adder in Verilog using Structural Modelling.

### SOFTWARE USED

Vivado 2018.3

### VERILOG CODE

```
`timescale 1ns/1ps


module VerilogAdder61(
    input [7:0] Ain,
    input [7:0] Bin,
    input Cin,
    output [8:0] Out
);
    wire[6:0] temp;
    FullAdder fa1(Ain[0], Bin[0], Cin, Out[0], temp[0]);
    FullAdder fa2(Ain[1], Bin[1], temp[0], Out[1], temp[1]);
    FullAdder fa3(Ain[2], Bin[2], temp[1], Out[2], temp[2]);
    FullAdder fa4(Ain[3], Bin[3], temp[2], Out[3], temp[3]);
    FullAdder fa5(Ain[4], Bin[4], temp[3], Out[4], temp[4]);
    FullAdder fa6(Ain[5], Bin[5], temp[4], Out[5], temp[5]);
    FullAdder fa7(Ain[6], Bin[6], temp[5], Out[6], temp[6]);
    FullAdder fa8(Ain[7], Bin[7], temp[6], Out[7], Out[8]);
Endmodule
```

### TESTBENCH


```
module AdderTestBench56;
    reg[7:0] Ain;
    reg[7:0] Bin;
    reg Cin;
    wire[8:0] Out;
    VerilogAdder44 a1(.Ain(Ain), .Bin(Bin), .Cin(Cin), .Out(Out));
    initial
    begin
        Cin = 1'b0 ;
        for (Ain = 0; Ain < 8'b11111111; Ain = Ain + 1) begin
            for (Bin = 0; Bin < 8'b11111111; Bin = Bin + 1) begin
                #10;
            end
            #10;
        end
    end
end
```

```
endmodule
```

## WAVE WINDOW OUTPUT

 

## SCHEMATIC

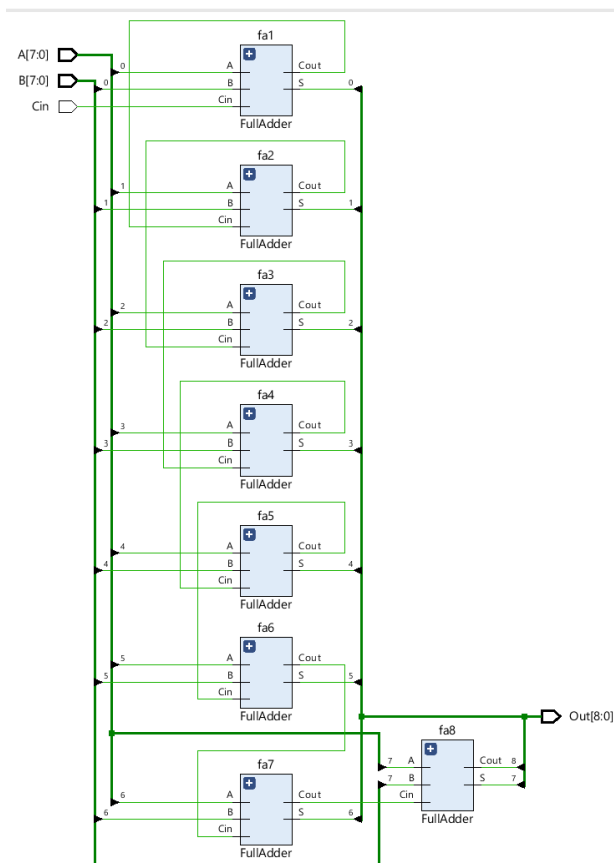

## CONCLUSION

Hence in this experiment, we successfully implemented an 8-bit adder using structural Verilog.

## **EXPERIMENT 04**

### **AIM**

In this experiment, our aim was to implement a 4-bit multiplier using structural Verilog.

### **SOFTWARE USED**

Vivado 2018.3

### **VERILOG CODE**

#### **XOR**

```
`timescale 1ns / 1ps

module VerilogXOR61 (
    input A8,
    input B9,
    input C0,
    output O2
);
    wire first1 ;
    xor(first1,A8,B9);
    xor(O2,first1,C0);
endmodule
```

#### **AND**

```
`timescale 1ns / 1ps

module AND61(
    input [3:0] An,
    input [3:0] Bn,
    output [3:0] Cn
);
    and(Cn[0],An[0],Bn[0]);
    and(Cn[1],An[1],Bn[1]);
    and(Cn[2],An[2],Bn[2]);
    and(Cn[3],An[3],Bn[3]);
endmodule
```

### **FULL ADDER WITH CARRY**

```
`timescale 1ns / 1ps

module VerilogCARRY61 (
    input Ae,
    input Be,
```

```

input Ce,
output Cout
);
wire w1, w2, w3, w4 ;
and(w1,Ae,Be);
and(w2,Ae,Ce);
and(w3,Be,Ce);
or(w4,w1,w2);
or(Cout,w4,w3);
endmodule

```

## STRUCTURAL ADDER

```

`timescale 1ns / 1ps

module VerilogFA61 (
    input Ao,
    input Bo,
    input Cin,
    output So,
    output Cout
);
    VerilogXOR61x1(Ao,Bo,Cin,So);
    VerilogCARRY61 FC1(Ao,Bo,Cin,Cout);
endmodule

```

## STRUCTURAL ADDER (4-BIT INPUT)

```

`timescale 1ns / 1ps

module VerilogADD44 (
    input [3:0] Ac,
    input [3:0] Bc,
    output Sc,
    output [3:0] Cout
);
    wire C0,C1,C2 ;
    VerilogFA61 fa1(Ac[0],Bc[0],Sc,C0);
    VerilogFA61 fa2(Ac[1],Bc[1],C0,Cout[0],C1);
    VerilogFA61 fa3(Ac[2],Bc[2],C1,Cout[1],C2);
    VerilogFA61 fa4(Ac[3],Bc[3],C2,Cout[2],Cout[3]);
endmodule

```

## MULTIPLIER

```

`timescale 1ns / 1ps

```


```

module VerilogMUL61 (
  input [3:0] Ar,
  input [3:0] Br,
  output [7:0] Pr
);
  wire [3:0] L0, L1, L2, L3 ;
  wire [3:0] C0, C1, C2, C3 ;
  AND4 a40({0,Ar[3],Ar[2],Ar[1]},{Br[0],Br[0],Br[0],Br[0]},L0);
  AND4 a41(Ar,{Br[1],Br[1],Br[1],Br[1]},L1);
  AND4 a42(Ar,{Br[2],Br[2],Br[2],Br[2]},L2);
  AND4 a43(Ar,{Br[3],Br[3],Br[3],Br[3]},L3);


  and a1(Pr[0],Ar[0],Br[0]);
  VerilogADD61 sa40(L0,L1,P[1],C0);
  VerilogADD61 sa41(L2,C0,P[2],C1);
  VerilogADD61 sa42(L3,C1,Pr[3],{Pr[7],Pr[6],Pr[5],Pr[4]});
endmodule

```

## WAVE WINDOW OUTPUT

 

## SCHEMATIC

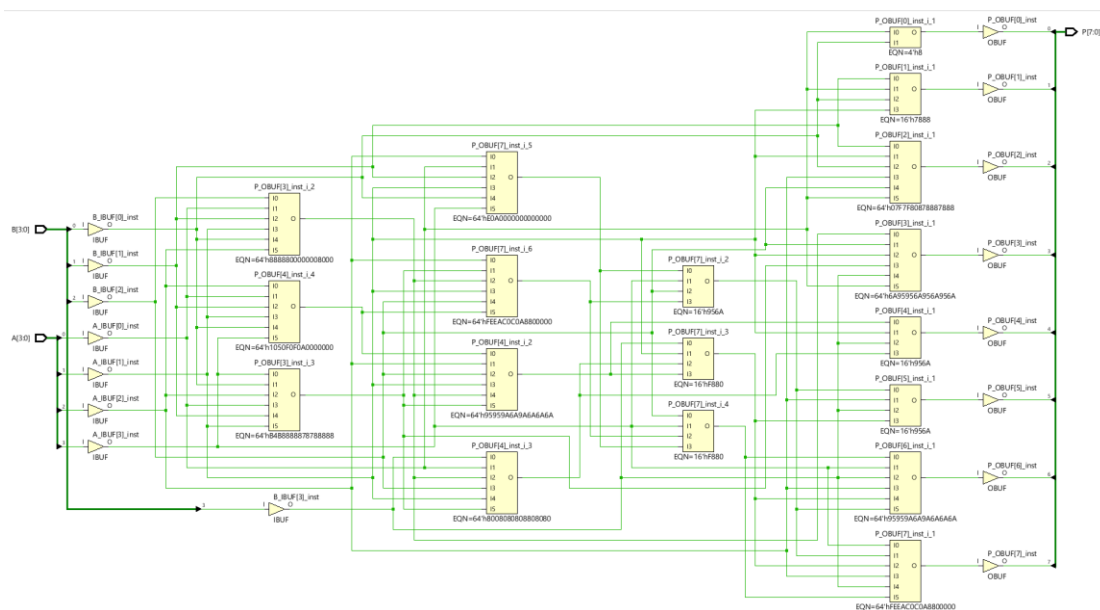

## CONCLUSION

Hence in this experiment, we successfully implemented a 4-bit multiplier using structural Verilog.



## **EXPERIMENT 05**

### **AIM**

In this experiment, our aim is to implement an 8:3 Encoder and a 3:8 Decoder in Verilog using Behavioral Modelling.

### **SOFTWARE USED**

Vivado 2018.3

### **VERILOG CODE**

#### **ENCODER 3:8**

```
`timescale 1ns / 1ps

module VerilogEnc61 (
    input [8:0] Yj,
    output reg [3:0] Outi
);
    always @(Yj) begin
        case(Yj)
            8'b00000001: Outi = 3'b000;
            8'b00000010: Outi = 3'b001;
            8'b00000100: Outi = 3'b010;
            8'b00001000: Outi = 3'b011;
            8'b00010000: Outi = 3'b100;
            8'b00100000: Outi = 3'b101;
            8'b01000000: Outi = 3'b110;
            8'b10000000: Outi = 3'b111;
            default: Outi = 3'bx;
        endcase
    end
endmodule
```

### **TEST BENCH**

```
`timescale 1ns / 1ps

module EncoderTestBench9;
    reg[7:0] Yj;
    wire[3:0] Outi;
    VerilogEnc61 enc(.Yj(Yj), .Outj(Outi));
    initial
    begin
        Y = 8'b00000001; #10;
        Y = 8'b00000010; #10;
        Y = 8'b00000100; #10;
    end
endmodule
```

```

Y = 8'b00001000; #10;
Y = 8'b00010000; #10;
Y = 8'b00100000; #10;
Y = 8'b01000000; #10;
Y = 8'b10000000; #10;
end
endmodule

```

### DECODER 8:3

```

`timescale 1ns / 1ps

module VerilogDec61 (
  input [2:0] Yi,
  output reg [7:0] Outj
);
  always @(Yi) begin
    case(Yi)
      3'b000: Outj = 8'b00000001;
      3'b001: Outj = 8'b00000010;
      3'b010: Outj = 8'b00000100;
      3'b011: Outj = 8'b00001000;
      3'b100: Outj = 8'b00010000;
      3'b101: Outj = 8'b00100000;
      3'b110: Outj = 8'b01000000;
      3'b111: Outj = 8'b10000000;
    endcase
  end
endmodule

```

### TEST BENCH

```

`timescale 1ns / 1ps

module DecoderTestBench12;
  reg [2:0] Yi;
  wire [7:0] Outj ;
  VerilogDec61 decod(.Yi(Yi), .Outj(Outj));
  initial begin
    Yi = 3'b000; #10;
    Yi = 3'b001; #10;
    Yi = 3'b010; #10;
    Yi = 3'b011; #10;
    Yi = 3'b100; #10;
    Yi = 3'b101; #10;

```


```

    Yi = 3'b110; #10;
    Yi = 3'b111; #10;
end
endmodule


```

## WAVE WINDOW OUTPUT

### ENCODER 3:8

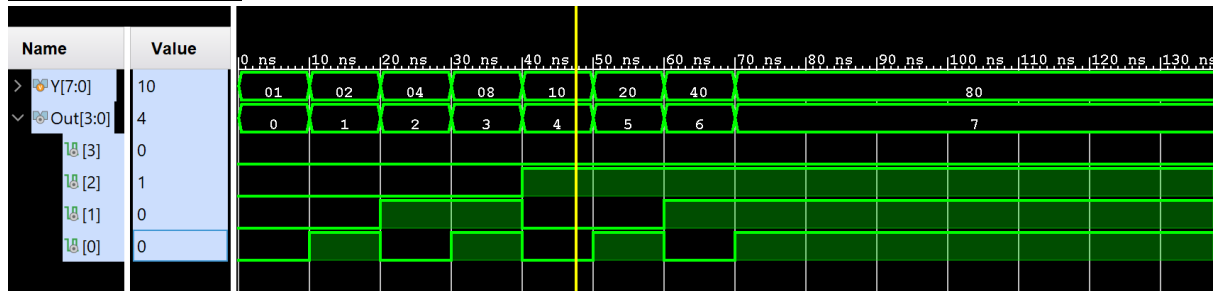


### DECODER 8:3

 


## SCHEMATIC

### ENCODER 3:8

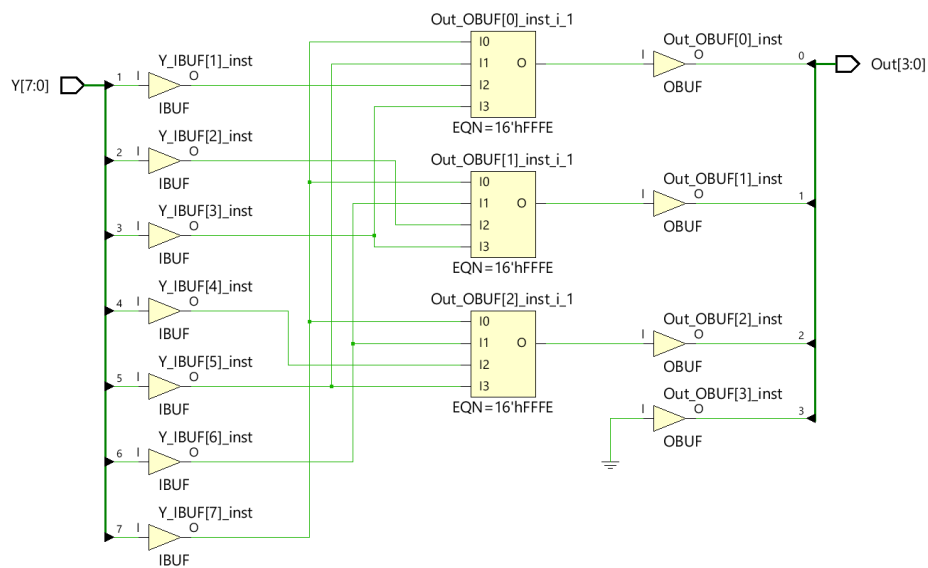

## DECODER 8:3

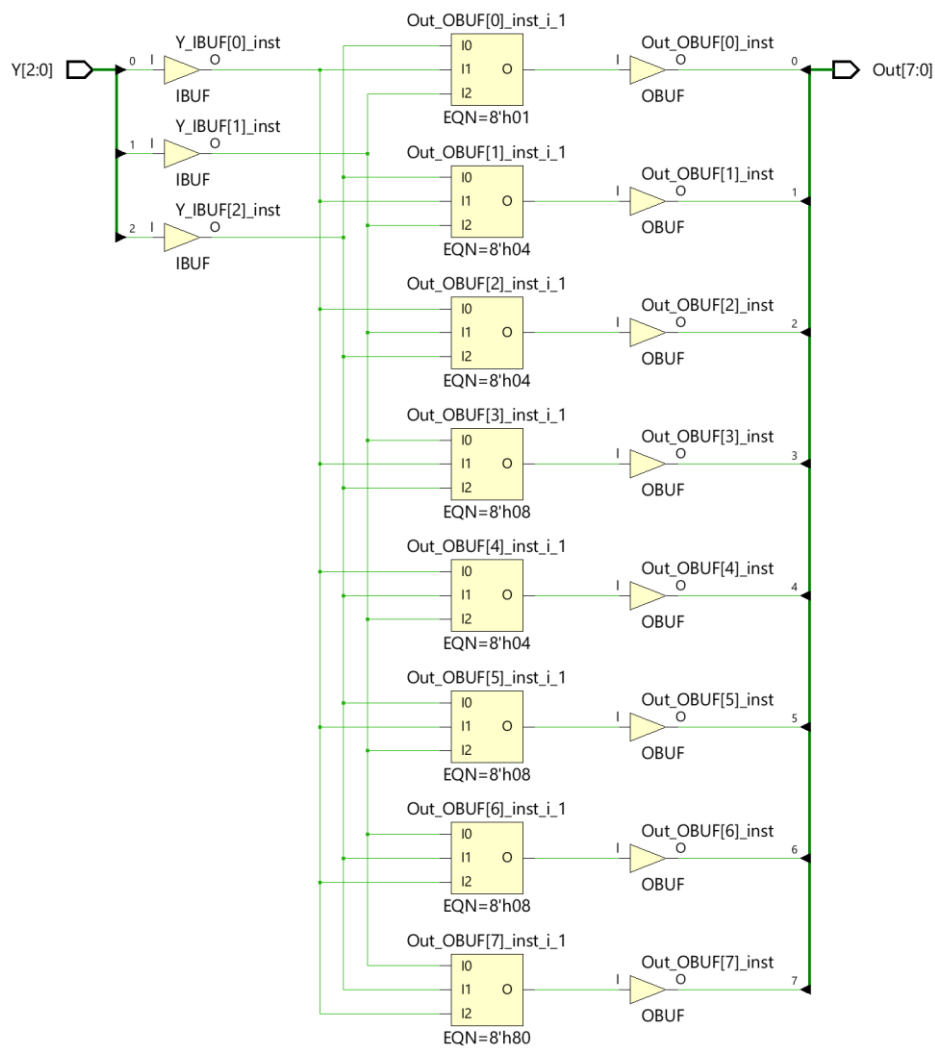

## CONCLUSION

Hence in this experiment, we successfully implemented a 3:8 Decoder and a n 8:3 Encoder using Behavioral Modelling in Verilog.

## **EXPERIMENT 06**

### **AIM**

In this experiment, our aim is to implement latches (SR Latch & D Latch) & Flip-Flops (JK Flip-Flop & T Flip-Flop) in Verilog using Behavioral Modelling.

### **SOFTWARE USED**

Vivado 2018.3

### **VERILOG CODE**

#### **SR LATCH**

```
`timescale 1ns / 1ps

module VerilogSR_LATCH61 (
    input Sn, Rm,
    output reg Q1, Q_not2
);
    always @ (Sn or Rm) begin
        if (Sn == 1 && Rm == 0) begin
            //Set
            Q1 = 1;
            Q_not2 = 0;
        end else if (Sn == 0 && Rm == 1) begin
            //Reset
            Q1 = 0;
            Q_not2 = 1;
        end else if (Sn == 0 && Rm == 0) begin
            //Hold State
            Q1 = Q1 ;
            Q_not2 = Q_not2 ;
        end else begin
            // invalid state
            Q1 = 1 ;
            Q_not2 = 1 ;
        end
    end
end
endmodule
```

### **TEST BENCH**

```
`timescale 1ns / 1ps

module SR_LatchTestBench6;
    reg Sn, Rm ;
    wire Q1, Q_not2;
```

```

VerilogSR_LATCH61 sr(Sn, Rm, Q1, Q_not2);
initial
begin
    Sn = 0;
    Rm = 0 ;
    repeat(4) begin
        #10 Sn = ~Sn;
        #10 Rm = ~Rm;
    end
    $stop;
end
endmodule

```

## D LATCH

```

`timescale 1ns / 1ps

module VerilogD_LATCH61 (
    input D1,
    input Eno,
    output reg Q2,
    output reg Q_not3
);
    always @ (D1 or Eno) begin
        if (Eno == 1) begin
            Q2 = D1;
            Q_not3 = ~D1 ;
        end
    end
end
endmodule

```

## TEST BENCH

```

`timescale 1ns / 1ps

module D_LatchTestBench1;
    reg D1, Eno;
    wire Q2, Q_not3;
    VerilogD_LATCH61 dl(D1, Eno, Q2, Q_not3);
    always #5 Eno = ~Eno;
    initial
    begin
        D1 = 0 ;
        Eno = 0;
        repeat(4) begin
            #10 D1 = ~D1 ;
        end
    end
endmodule

```

```

    $stop;
end
endmodule

```

## JK FLIP FLOP

```

`timescale 1ns / 1ps

module VerilogJK_LATCH61 (
    input Ji,
    input Ki,
    input clk,
    output reg Qi,
    output reg Q_not1
);
    always @(posedge clk) begin
        if(Ji == 0 && Ki == 1) begin
            Qi = 0 ;
            Q_not1 = 1 ;
        end else if(Ji == 1 && Ki == 0) begin
            Qi = 1 ;
            Q_not1 = 0 ;
        end else if(Ji == 1 && Ki == 1) begin
            Qi = ~Qi;
            Q_not1 = ~Qi ;
        end
    end
end
endmodule

```

## TEST BENCH

```

`timescale 1ns / 1ps

module JKFlipFlopTestBench13;
    reg Ji Ki, clk ;
    wire Qi, Q_not1;
    VerilogJK_LATCH61 jk(Ji, Ki, clk, Qi, Q_not1);
    always #5 clk = ~clk ;
    initial
        begin
            Ji = 0 ;
            Ki = 0 ;
            clk = 0 ;
            repeat(8) begin
                #10 Ji = ~Ji ;
                #10 Ki = ~Ki ;
            end
        end
    $stop;
endmodule

```

```
end
endmodule
```

## T FLIP FLOP

```
`timescale 1ns / 1ps

module VerilogT_LATCH61 (
    input Tn,
    input clk,
    output reg Q1,
    output reg Q_not2
);
    initial begin
        Q1 = 0 ;
        Q_not2 = 1 ;
    end
    always @(posedge clk) begin
        if(Tn == 1) begin
            Q1 = ~Q1 ;
            Q_not2 = ~Q_not2 ;
        end
    end
endmodule
```

## TEST BENCH


```
`timescale 1ns / 1ps

module TFlipFlopTestBench14;
    reg Tn, clk ;
    wire Q1, Q_not2 ;
    VerilogT_LATCH61 T1(.Tn(Tn), .clk(clk), .Q1(Q1), .Q_not2(Q_not2));
    always #5 clk = ~clk ;
    initial begin
        Tn = 0 ;
        clk = 0 ;
        repeat(4) begin
            #10 ;
            Tn = ~Tn ;
        end
    end
endmodule
```




WAVE WINDOW OUTPUT


SR LATCH

 


D LATCH

 

JK FLIP FLOP

 


T FLIP FLOP

 


SCHEMATIC


SR LATCH

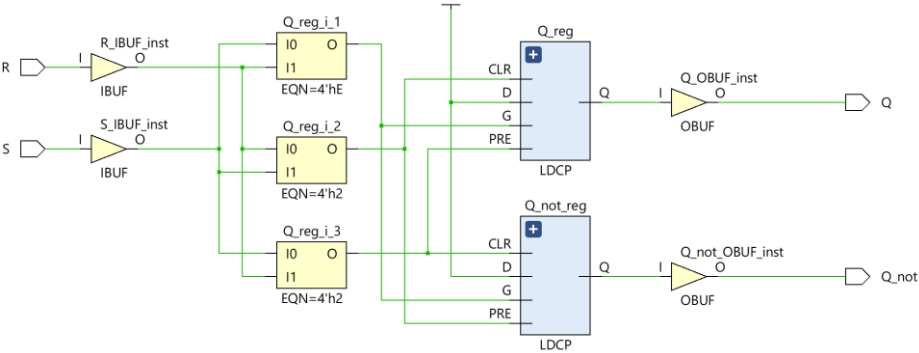


## D LATCH

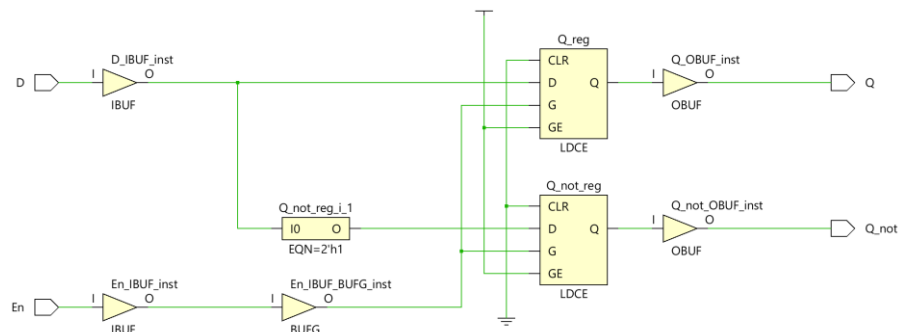

## JK FLIP FLOP

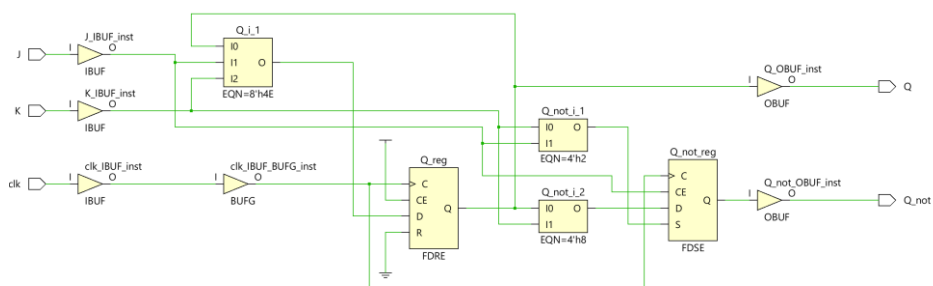

## T FLIP FLOP

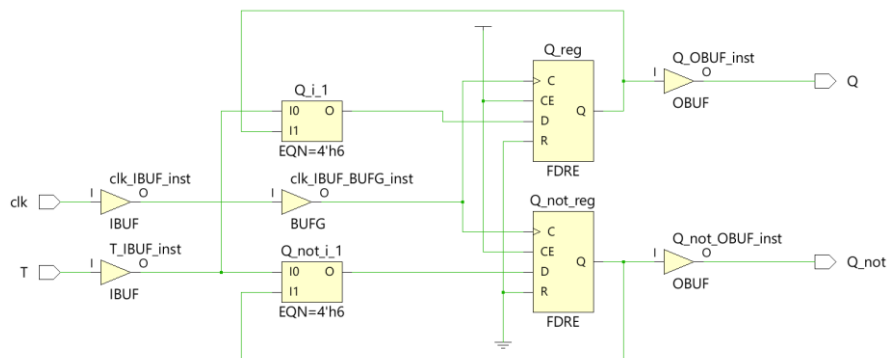

## CONCLUSION

Hence in this experiment, we successfully implemented Latches and Flip Flops using Behavioral Modelling in Verilog.

## **EXPERIMENT 07**

### **AIM**

In this experiment, our aim is to implement Shift Registers (SISO, SIPO, PISO & PIPO) in Verilog.

### **SOFTWARE USED**

Vivado 2018.3

### **VERILOG CODE**

#### **SISO REGISTER**

```
`timescale 1ns / 1ps

module VerilogSISO_61 (
    input In,
    input clk,
    input clear,
    output Out
);
    reg [3:0] temp ;
    always @ (posedge clk)
    begin
        if(clear)
            temp <= 4'b0000;
        else
            temp <= {temp[2:0], In};
    end
    assign Out = temp[3];
endmodule
```

### **TEST BENCH**

```
`timescale 1ns / 1ps

module SISO6TestBench;
    reg In, clk, clear;
    wire Out ;
    VerilogSISO_61 s4(.In(In), .clk(clk), .clear(clear), .Out(Out));
    always #10 clk = ~clk ;
    initial
    begin
        clk = 0;
        In = 1;
        clear = 0;
        repeat(32) begin
            In = ~In ;
            #20;
        end
    end
```

```

    end
    $stop;
end
endmodule

```

## SIPO SHIFT REGISTER

```

`timescale 1ns / 1ps

module VerilogSIPO_61 (
    input In,
    input clk,
    input clear,
    output [3:0] Out
);
    reg [3:0] temp ;
    always @ (posedge clk)
    begin
        if(clear)
            temp <= 4'b0000;
        else
            temp <= {temp[2:0], In};
    end
    assign Out = temp;
endmodule

```

## TEST BENCH

```

`timescale 1ns / 1ps

module SIPO4TestBench;
    reg In, clk, clear;
    wire[3:0] Out ;
    VerilogSIPO_61 s4(.In(In), .clk(clk), .clear(clear), .Out(Out));
    always #10 clk = ~clk ;
    initial
    begin
        clk = 0;
        In = 1;
        clear = 0;
        repeat(32) begin
            In = ~In ;
            #20;
        end
    end
    $stop;
end
endmodule

```

### PISO SHIFT REGISTER (4-BIT)

```
`timescale 1ns / 1ps

module VerilogPISO_61 (
    input [3:0] In,
    input clk,
    input load,
    output reg Out
);
    reg [3:0] temp ;
    always @(posedge clk) begin
        if(load)
            temp = In ;
        else
            temp = {temp[2:0], 1'b0} ;
        Out = temp[3] ;
    end
endmodule
```

### TEST BENCH

```
`timescale 1ns / 1ps

module PISO4TestBench;
    reg [3:0] In;
    reg clk, load;
    wire Out ;
    VerilogPISO_61 p4(.In(In), .clk(clk), .load(load), .Out(Out));
    always #10 clk = ~clk ;
    initial
        begin
            clk = 0;
            In = 4'b0111; load = 1 ; #20;
            load = 0 ; #80
            In = 4'b1010; load = 1 ; #20 ;
            load = 0 ; #80
            In = 4'b0101 ; load = 1 ; #20;
            load = 0 ; #80;
            $stop;
        end
endmodule
```

### PIPO SHIFT REGISTER (4-BIT)

```
`timescale 1ns / 1ps

module VerilogPIPO_61 (
    input [3:0] In,
    input clk,
```

```

input reset,
output reg [3:0] Out
);
always @ (posedge clk or negedge reset)
begin
    if (~reset)
        Out <= 4'b0000;
    else
        Out <= {Out[2:0], In};
    end
endmodule

```

## TEST BENCH

```


`timescale 1ns / 1ps

module PIPO4TestBench;
reg [3:0] In;
reg clk, reset;
wire[3:0] Out ;
VerilogPIPO_61 p4(.In(In), .clk(clk), .reset(reset), .Out(Out));
always #10 clk = ~clk ;
initial
begin
    clk = 0;
    reset = 1 ;
    In = 4'b0101 ; #40 ;
    reset = 0; #10 ;
    reset = 1 ; In = 4'b1111; #40 ;
    In = 4'b1010; #40 ;
    $stop;
end
endmodule


```

## WAVE WINDOW OUTPUT


### SISO SHIFT REGISTER (4-BIT)

 


### SIPO SHIFT REGISTER (4-BIT)

 

### PISO SHIFT REGISTER (4-BIT)

 


### PIPO SHIFT REGISTER (4-BIT)

 


## SCHEMATIC


### SISO SHIFT REGISTER (4-BIT)

 


### SIPO SHIFT REGISTER (4-BIT)

 

## PISO SHIFT REGISTER (4-BIT)

 

## PIPO SHIFT REGISTER (4-BIT)

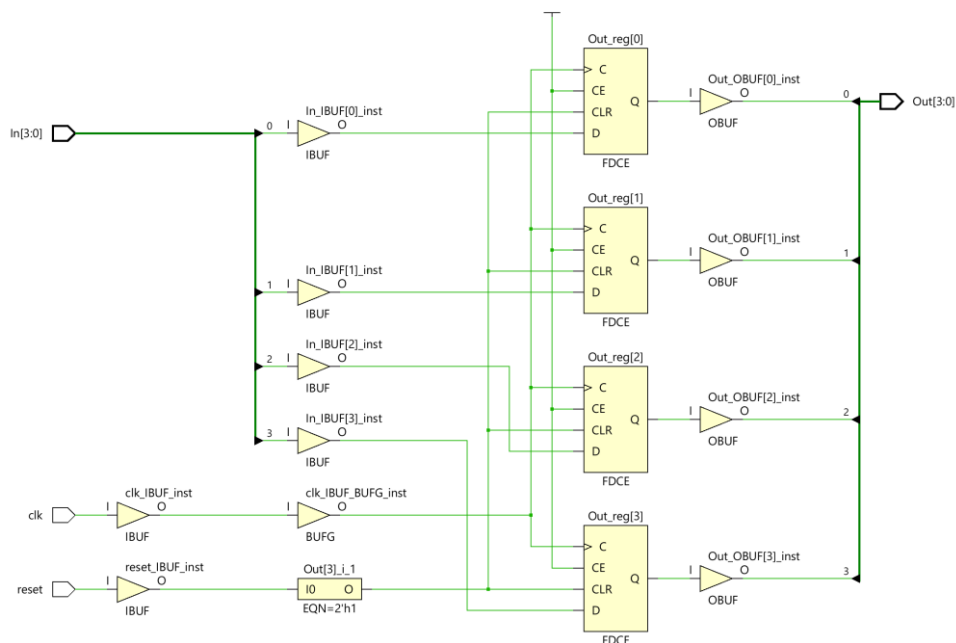

## CONCLUSION

Hence in this experiment, we successfully implemented 4-bit Shift Registers in Verilog.



## **EXPERIMENT 08**

### **AIM**

In this experiment, our aim is to implement a Universal Shift Register in Verilog.

### **SOFTWARE USED**

Vivado 2018.3

### **VERILOG CODE**

```
`timescale 1ns / 1ps

module SHIFT_REG61 (
    input [3:0] In,
    input clk,
    input reset,
    input left_shift,
    input right_shift,
    output reg [3:0] Out
);
    reg [3:0] shift_reg;
    always @(posedge clk) begin
        if (~reset) begin
            shift_reg <= 4'b0;
        end else begin
            if (left_shift) begin
                //Left Shift
                shift_reg <= {shift_reg[2:0], In};
            end else if (right_shift) begin
                //Right Shift
                shift_reg <= {In, shift_reg[3:1]};
            end else begin
                //Parallel Loading
                shift_reg <= In;
            end
        end
        Out = shift_reg;
    end
endmodule
```

### **TEST BENCH**

```
`timescale 1ns / 1ps


module UniversalShiftRegisterTestBench78;
    reg [3:0] In;
    reg clk;
```

```


reg reset;
reg left_shift;
reg right_shift;
wire [3:0] Out;
SHIFT_REG61 usr(
    .In(In), .clk(clk), .reset(reset), .left_shift(left_shift),
    .right_shift(right_shift), .Out(Out));
initial begin
    clk = 0;
    forever #5 clk = ~clk;
end
initial begin
    reset = 1;
    In = 4'b0;
    left_shift = 0;
    right_shift = 0;
    #10 In = 4'b1010;
    #10 left_shift = 1;
    #10 left_shift = 0;
    #10 right_shift = 1;
    #10 right_shift = 0;
    #10 $finish;
end
endmodule

```

## WAVE WINDOW OUTPUT

 

## SCHEMATIC

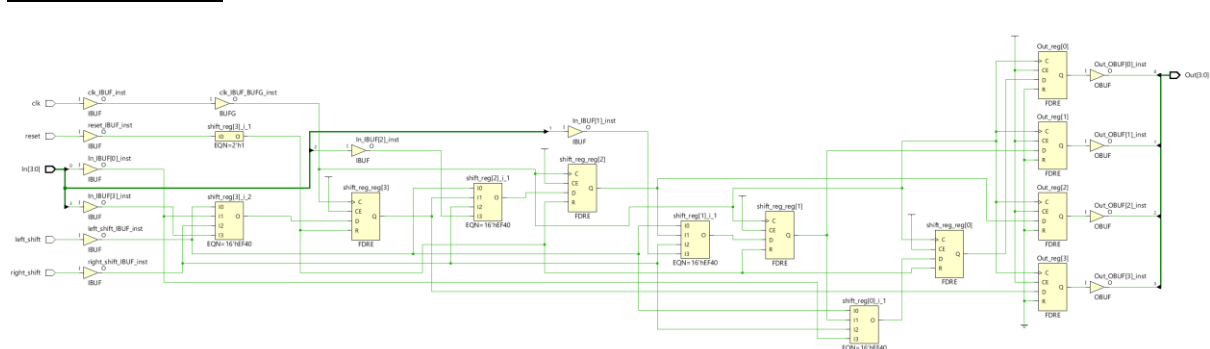

## CONCLUSION

Hence in this experiment, we successfully implemented a 4-bit Bi-directional Universal Shift Register in Verilog.

## **EXPERIMENT 09**

### **AIM**

In this experiment, our aim is to implement 4-bit Counters (Synchronous Up & Down) in Verilog.

### **SOFTWARE USED**

Vivado 2018.3

### **VERILOG CODE**

#### **SYNCHRONOUS UP COUNTER (4-BIT)**

```
`timescale 1ns / 1ps

module UP_COUNTER61 (
    input clk1,
    input reset1,
    output reg [3:0] Out1
);
    always @(posedge clk1 or posedge reset1) begin
        if (reset1) begin
            Out1 <= 4'b0000;
        end else begin
            Out1 <= Out + 1;
        end
    end
endmodule
```

### **TEST BENCH**

```
`timescale 1ns / 1ps

module UpCounterTestBench56;
    reg clk1, reset1;
    wire [3:0] Out1;
    UP_COUNTER61 up(.clk1(clk1), .reset1(reset1), .Out1(Out1));
    always #5 clk1 = ~clk1 ;
    initial begin
        clk1 = 0 ;
        reset1 = 1 ;
        #5 reset1 = 0 ;
    end
endmodule
```

#### **SYNCHRONOUS DOWN COUNTER (4-BIT)**

```
`timescale 1ns / 1ps
```

```

module DOWN_COUNTER61 (
    input clk1,
    input reset1,
    output reg [3:0] Out1
);
always @(posedge clk1 or posedge reset1) begin
    if (reset1) begin
        Out1 <= 4'b0000;
    end else begin
        Out1 <= Out1 - 1;
    end
end
endmodule

```

## TEST BENCH

```


`timescale 1ns / 1ps

module DownCounterTestBench34;
    reg clk1, reset1;
    wire [3:0] Out1 ;
    DOWN_COUNTER61 down(.clk1(clk1), .reset1(reset1), .Out1(Out1));
    always #5 clk1 = ~clk1 ;
    initial begin
        clk1 = 0 ;
        reset1 = 1 ;
        #5 reset1 = 0 ;
    end
endmodule


```

## WAVE WINDOW OUTPUT

### SYNCHRONOUS UP COUNTER (4-BIT)

 


### SYNCHRONOUS DOWN COUNTER (4-BIT)

 


## SCHEMATIC

### SYNCHRONOUS UP COUNTER (4-BIT)

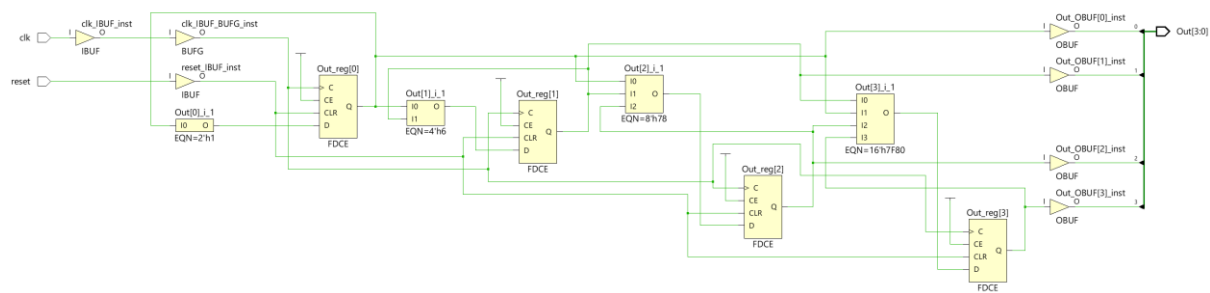

### SYNCHRONOUS DOWN COUNTER (4-BIT)

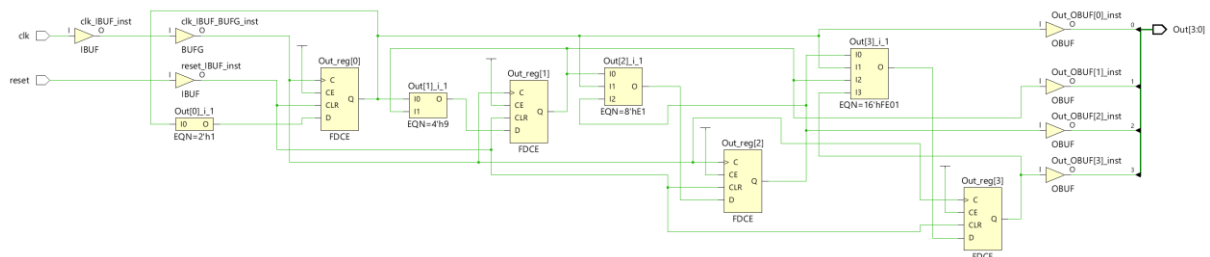

## CONCLUSION

Hence in this experiment, we successfully implemented Synchronous Up/Down Counters in Verilog.

## **EXPERIMENT 10**

### **AIM**

In this experiment, our aim is to implement a PRBS (Pseudo Random Binary Sequence) Generator in Verilog.

### **SOFTWARE USED**

Vivado 2018.3

### **VERILOG CODE**

#### **PRBS GENERATOR**

This generator uses an 8-bit feedback shift register and the feedback polynomial is  $x_7 + x_6 + 1$ .

```
`timescale 1ns / 1ps

module PRBS_GEN_61 (
    input clk1,
    input reset1,
    output Out1
);
    reg [7:0] shift_reg;
    wire feedback = shift_reg[7] ^ shift_reg[6];

    always @(posedge clk1 or posedge reset1) begin
        if (reset1) begin
            shift_reg <= 8'b00000001;
        end else begin
            shift_reg <= {shift_reg[6:0], feedback};
        end
    end
    assign Out1 = shift_reg[0];
endmodule
```

### **TEST BENCH**

```
`timescale 1ns / 1ps

module PRBSTestBench123;
    reg clk, reset;
    wire Out ;
    PRBS_GEN_61 prbs(.clk1(clk1), .reset1(reset1), .Out1(Out1));
    initial begin
        clk1 = 0;
        forever #5 clk1 = ~clk1;
    end
end
```

Name	Value
clk	0
reset	0
Out	1

The timing diagram shows three signals over a 900 ns period. The clock (clk) is a periodic square wave. The reset signal is a single pulse at the beginning. The output (Out) is a square wave that changes state at various points, including when reset is active and at several clock edges.

[illegible]

Hence in this experiment, we successfully implemented a PRBS using a custom feedback polynomial and an 8-bit shift register in Verilog.